

Name: \_\_\_\_\_

Write your responses on the extra paper provided. Hand in this exam paper along with your solutions, please place your name on the top of each page. Show all of your work.

## 1 Short Answer


Answer all of the following questions, each is worth 10 points.

1. Draw a diagram for the von Neumann model of a uniprocessor computer.
2. State Moore's Law and the modified version of Moore's Law.
3. Convert the hexadecimal number  $A67FD1$  to both binary and octal.
4. Compute  $A67FD1 + B12AC$  and  $A67FD1 - B12AC$ , give your answer in hexadecimal.
5. Find the 2's complement of 0111010011000000, the most significant bit is the sign bit.
6. Using just NAND gates, construct the circuits for the AND, OR, and NOT gates.
7. Construct the truth tale for both the half adder and the full adder. Also, give their logical expressions.
8. Given the following truth table, write the logical experssion for the table in both canonical SOP and POS forms. Then using the SOP form, construct the circuit for this table.

$A$	$B$	$C$	$P$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

9. Take the truth table from the previous exercise, construct the K-Map for this table, give the reduced logical expression, and draw the minimized circuit.
10. Draw the circuit diagram, in the gate form, for a clocked  $SR$  flip-flop.
11. Using clocked  $JK$  flip-flops, construct a 4-bit counter.
12. Using clocked  $D$  flip-flops, construct a 4-bit register.

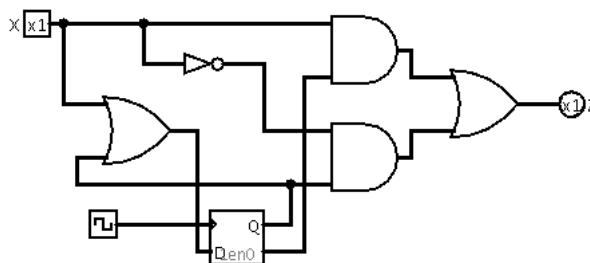13. For the following sequential circuit, give the next-state, output, and transition tables. Also draw the state diagram for the circuit. The flip-flop in the circuit is a *D* flip-flop.



14. Give the output of the following NASM program, named `final`, given the input of `./final 1 2 3 4 5 6 7 8 9 10`

The subroutines `atoi`, `itoa`, `iprint`, `iprintLF`, `sprint`, `sprintLF`, `slen`, and `quit` are from the `%include 'functions.asm'` at the beginning, and are those we went over in class.

```

1  %include 'functions.asm'      42      call    iprintLF      83      jmp     loop
2                                43                                84
3  SECTION .data                44      mov     eax, [n]      85 done:
4  msg1 db 'Contents: ', 0h     45      mov     ecx, 2      86      call    writearray
5  msg2 db ' ', 0h              46      mov     edx, 0      87
6                                47      div     ecx      88 finish:
7  SECTION .bss                 48      mov     ecx, eax      89      call    quit
8  n resd 1                     49      mov     esi, 0      90
9  m resd 1                     50      mov     ebx, A      91 writearray:
10 A resd 100                    51      mov     edx, A      92      push    eax
11                                52                                93      push    ebx
12 SECTION .text                53      mov     eax, [n]      94      push    ecx
13 global _start                 54      mov     edx, 1      95      push    edx
14                                55      sub     eax, edx      96
15 _start:                      56      mov     edx, 4      97      mov     ecx, [n]
16      pop     ecx               57      mul     edx      98      mov     edx, A
17      cmp     ecx, 1            58      add     eax, A      99      mov     eax, msg1
18      je      finish           59      mov     edx, eax      100     call    sprint
19      dec     ecx               60                                101
20      mov     [n], ecx          61 loop:                102 .writeloop:
21                                62      cmp     esi, ecx      103     cmp     ecx, 0
22      pop     eax               63      je      done        104     je      .return
23      mov     edx, A            64      call    writearray      105     mov     eax, [edx]
24                                65                                106     call    iprint
25 readloop:                     66      mov     eax, [ebx]      107     mov     eax, msg2
26      cmp     ecx, 0            67      mov     edi, [edx]      108     call    sprint
27      je      DoSomething       68      mov     [edx], eax      109
28      pop     eax               69      mov     [ebx], edi      110     add     edx, 4
29      call    atoi              70      add     ebx, 4      111     dec     ecx
30      mov     [edx], eax        71      add     ebx, 4      112     jmp     .writeloop
31      add     edx, 4            72      mov     eax, edx      113
32                                73      mov     edi, 16      114 .return:
33      dec     ecx               74      add     eax, edi      115     mov     eax, msg2
34      jmp     readloop          75      mov     edi, [m]      116     call    sprintLF
35                                76      mov     edx, 0      117
36 DoSomething:                  77      div     edi      118     pop     edx
37      mov     eax, [n]          78      mov     eax, A      119     pop     ecx
38      mov     edx, 4            79      add     eax, edx      120     pop     ebx
39      mul     edx               80      mov     edx, eax      121     pop     eax
40      mov     [m], eax          81                                122
41                                82      inc     esi      123     ret

```

15. For each of the following, state the name of the type of addressing used in the command.

- (a) LDA Z
- (b) LDA\* Z, 3
- (c) LDA Z, 1
- (d) LDA\* Z

16. For each of the following load functions, give the effective address of the memory location being addressed and the contents of the accumulator resulting from the command. Assume that the contents of memory and the index registers are as follows and that all indirect indexing mode addresses are preindexed. Also, the symbol Z has value C and Y has value 11, both in hexadecimal. Memory and register contents are also in hexadecimal.

Address	Contents
0	4
1	E
2	3
3	12
4	A
5	2
6	5
7	10
8	C
9	A
A	3
B	5
C	7
D	1
E	0
F	0
10	0
11	AA
12	1D
13	3
14	5
15	C1
16	D
17	8
18	2
19	F
1A	9
1B	E

Index Register	Contents
1	A
2	7
3	4

(a) LDA Y

Address	Accumulator

(b) LDA\* Z

Address	Accumulator

(c) LDA\* Y, 2

Address	Accumulator

(d) LDA\* Z, 3

Address	Accumulator


(e) LDA Z, 1

Address	Accumulator


## 2 Circuit Analysis

Do one and only one of the following exercises. This question is worth 50 points.

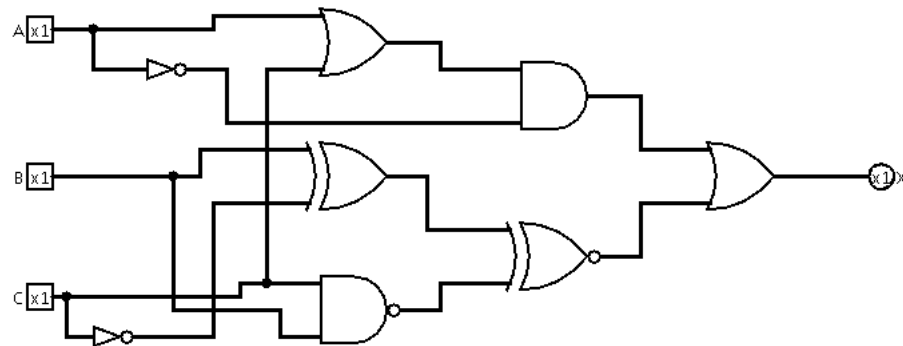17. Do the following for the circuit below.



- Construct the truth table for the circuit.
  - Write the circuit's logical function in canonical SOP form.
  - Write the circuit in minterm form.
  - Write the circuit in maxterm form.
  - Write the K-Map for the circuit, show the groupings you would use, and then construct the minimized logical circuit function in SOP form.
  - Using the K-Map work, write the circuit diagram of the minimized circuit.
18. For the following circuit, the top flip-flop is a  $T$  flip-flop and the bottom flip-flop is a  $JK$  flip-flop.

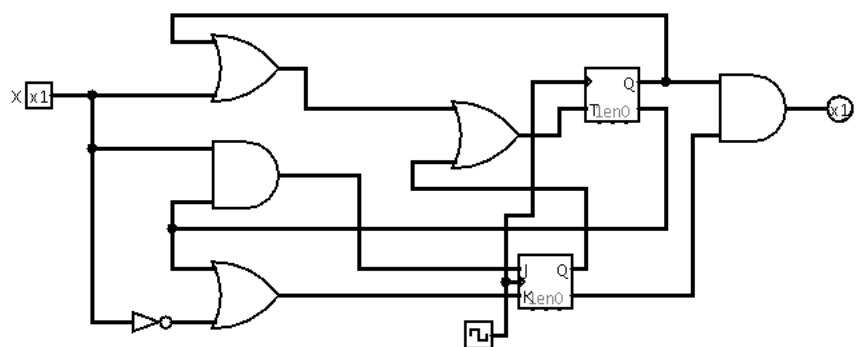

- Create the transition tables for the two flip-flops.
- Create the transition table.
- Create the next state table.
- Create the output table.
- Create the next state/output table.
- Create the state diagram.

### Flip-Flop Characteristic Tables

$Q(t)$	$SR$	$Q(t+1)$
0	00	0
0	01	0
0	10	1
0	11	—
1	00	1
1	01	0
1	10	1
1	11	—

$Q(t)$	$JK$	$Q(t+1)$
0	00	0
0	01	0
0	10	1
0	11	1
1	00	1
1	01	0
1	10	1
1	11	0

$Q(t)$	$D$	$Q(t+1)$
0	0	0
0	1	1
1	0	0
1	1	1

$Q(t)$	$T$	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

### Flip-Flop Excitation Tables

$Q(t)$	$Q(t+1)$	$SR$	$D$	$JK$	$T$
0	0	0d	0	0d	0
0	1	10	1	1d	1
1	0	01	0	d1	1
1	1	d0	1	d0	0